



Lecture 3 – Logic Gate Level Minimization

Lan-Da Van (范倫達), Ph. D.
Department of Computer Science
National Chiao Tung University
Taiwan, R.O.C.
Fall, 2007

Source: Charles Kime & Thomas Kaminski

© 2004 Pearson Education, Inc.

[Terms of Use](#)


(Hyperlinks are active in View Show mode)



Outline

Lecture 3

 - **Circuit Optimization**
 - **Two-Level Optimization**
 - **Map Manipulation**
 - **Multi-Level Circuit Optimization**
- **Additional Gates and Circuits**
 - **Other Gate Types**
 - **Exclusive-OR Operator and Gates**
 - **High-Impedance Outputs**






Circuit Optimization

Lecture 3

 
- Goal: To obtain the simplest implementation for a given function
- Optimization is a more formal approach to simplification that is performed using a specific procedure or algorithm
- Optimization requires a cost criterion to measure the simplicity of a circuit
- Three distinct cost criteria will be used:
 - Literal cost (L)
 - Gate input cost (G)
 - Gate input cost with NOTs (GN)





Literal Cost


- Literal – a variable or its complement
- Literal cost – the number of literal appearances in a Boolean expression corresponding to the logic circuit diagram
- Examples:
 - $F = BD + A\bar{B}C + A\bar{C}\bar{D}$ $L = 8$
 - $F = BD + A\bar{B}C + A\bar{B}\bar{D} + AB\bar{C}$ $L = 11$
 - $F = (A + B)(A + D)(B + C + \bar{D})(\bar{B} + \bar{C} + D)$ $L = 10$
 - Which solution is best? (first verify the equality)

 



Gate Input Cost


- Gate input costs - the number of inputs to the gates in the implementation corresponding exactly to the given equation or equations. (G - inverters not counted, GN - inverters counted)
- For SOP and POS equations, it can be found from the equation(s) by finding the sum of:
 - all literal appearances
 - the number of terms excluding terms consisting only of a single literal, (G) and
 - optionally, the number of distinct complemented single literals (GN).
- Example: which solution is best ?
 - $F = BD + A\bar{B}C + A\bar{C}\bar{D}$ $G = 11, GN = 14$
 - $F = BD + A\bar{B}C + A\bar{B}\bar{D} + ABC\bar{C}$ $G = 15, GN = 19$
 - $F = (A + B)(A + D)(B + C + \bar{D})(\bar{B} + \bar{C} + D)$ $G = 14, GN = 17$

 




Cost Criteria (1/2)

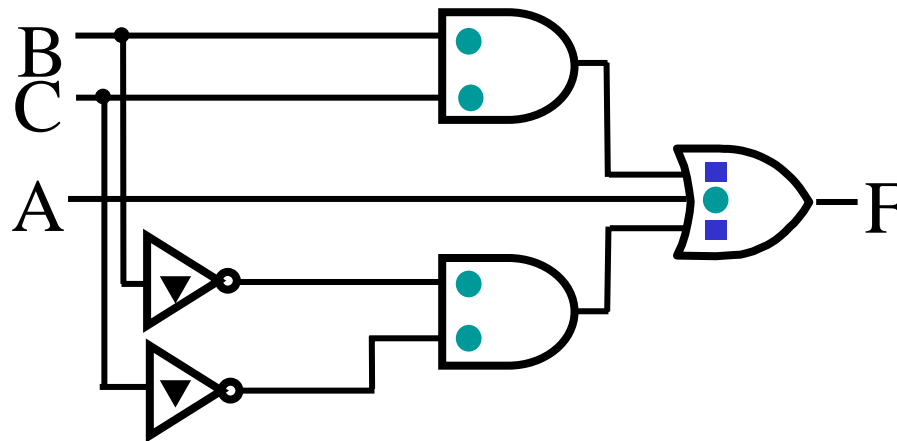- **Example 1:** $\nabla \nabla$ $GN = G + 2 = 9$
- $F = \overset{\bullet}{A} + \overset{\bullet}{B} \underset{\blacksquare}{C} + \overset{\bullet}{\bar{B}} \overset{\bullet}{\bar{C}}$ $L = 5$
- $G = L + 2 = 7$




 
- **L (literal count)** counts the AND inputs and the single literal OR input.
- **G (gate input count)** adds the remaining OR gate inputs
- **GN (gate input count with NOTs)** adds the inverter inputs





Cost Criteria (2/2)

  - **Example 2:**
- **$F = A B C + \bar{A}\bar{B}\bar{C}$**
- **$L = 6 \quad G = 8 \quad GN = 11$**
- **$F = (A + \bar{C})(\bar{B} + C)(\bar{A} + B)$**
- **$L = 6 \quad G = 9 \quad GN = 12$**
- **Same function and same literal cost**
- **But first circuit has better gate input count and better gate input count with NOTs**
- **Select the former design!**






Boolean Function Optimization

Lecture 3

- Minimizing the gate input (or literal) cost of a (a set of) Boolean equation(s) is to reduce the circuit cost.
- We choose gate input cost.
- Boolean algebra and graphical techniques are tools to minimize cost criteria values.
- Some important questions:
 - When do we stop trying to reduce the cost?
 - Do we know when we have a minimum cost?
- Treat optimum or near-optimum cost functions for two-level (SOP and POS) circuits first.
- Introduce a graphical technique using Karnaugh maps (K-maps, for short)

 




Karnaugh Maps (K-map)

Lecture 3

- A K-map is a collection of squares
 - Each square represents a minterm
 - The collection of squares is a graphical representation of a Boolean function
 - Adjacent squares differ in the value of **one** variable
 - Alternative algebraic expressions for the same function are derived by recognizing patterns of squares
- The K-map can be viewed as
 - A reorganized version of the truth table
 - A topologically-warped Venn diagram as used to visualize sets in algebra of sets

 




Some Uses of K-Maps

Lecture 3

 - Provide a means for:
 - Finding optimum or near optimum
 - SOP and POS standard forms, and
 - two-level AND/OR and OR/AND circuit implementations
 - for functions with small numbers of variables
 - Visualizing concepts related to manipulating Boolean expressions, and
 - Demonstrating concepts used by computer-aided design programs to simplify large circuits






Two Variable Maps

- A 2-variable Karnaugh Map:
 - Note that minterm m_0 and minterm m_1 are “adjacent” and differ in the value of the variable y
 - Similarly, minterm m_0 and minterm m_2 differ in the x variable.
 - Also, m_1 and m_3 differ in the x variable as well.
 - Finally, m_2 and m_3 differ in the value of the variable y .

	$y = 0$	$y = 1$
$x = 0$	$m_0 =$ $\bar{x}\bar{y}$	$m_1 =$ $\bar{x}y$
$x = 1$	$m_2 =$ xy	$m_3 =$ $x\bar{y}$

 



K-Map and Truth Tables


- The K-Map is just a different form of the truth table.
- Example – Two variable function:
 - We choose a,b,c and d from the set {0,1} to implement a particular function, $F(x,y)$.

Function Table

Input Values (x,y)	Function Value $F(x,y)$
0 0	a
0 1	b
1 0	c
1 1	d

K-Map

	y = 0	y = 1
x = 0	a	b
x = 1	c	d

 



K-Map Function Representation


Lecture 3

- Example: $F(x,y) = x$

$F = x$	$y = 0$	$y = 1$
$x = 0$	0	0
$x = 1$	1	1

- For function $F(x,y)$, the two adjacent cells containing 1's can be combined using the Minimization Theorem:

$$F(x,y) = x\bar{y} + xy = x$$

 



K-Map Function Representation

Lecture 3


- Example: $G(x,y) = x + y$

$G = x+y$	$y = 0$	$y = 1$
$x = 0$	0	1
$x = 1$	1	1

- For $G(x,y)$, two pairs of adjacent cells containing 1's can be combined using the Minimization Theorem:

$$G(x,y) = (\overline{x}\overline{y} + x\overline{y}) + (xy + \overline{x}y) = x + y$$

Duplicate xy

 



Three Variable Maps


- A three-variable K-map:

	yz=00	yz=01	yz=11	yz=10
x=0	m₀	m₁	m₃	m₂
x=1	m₄	m₅	m₇	m₆

- Where each minterm corresponds to the product terms:

	yz=00	yz=01	yz=11	yz=10
x=0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}yz$	$\bar{x}y\bar{z}$
x=1	$x\bar{y}\bar{z}$	$x\bar{y}z$	xyz	$xy\bar{z}$

 - Note that if the binary value for an index differs in one bit position, the minterms are adjacent on the K-Map






Alternative Map Labeling

- Map use largely involves:
 - Entering values into the map, and
 - Reading off product terms from the map.
- Alternate labelings are useful:

	\bar{y}	y		
\bar{x}	0	1	3	2
x	4	5	7	6
	\bar{z}	z	\bar{z}	

	y	z	y	
	00	01	11	10
0	0	1	3	2
1	4	5	7	6
	z			

 



Example Functions

- By convention, we represent the minterms of F by a "1" in the map and leave the minterms of \bar{F} blank

- Example:

$$F(x, y, z) = \Sigma_m(2,3,4,5)$$

$$F(x,y,z)=?$$


		y	
	0	1	3
	1		2
x	4	5	7
	1	1	6

- Example:

$$G(a, b, c) = \Sigma_m(3,4,6,7)$$

- Learn the locations of the 8 indices based on the variable order shown (x, most significant and z, least significant) on the map boundaries

		z	
	0	1	3
	1		2
a	4	5	7
	1		1
			6
		c	

 




Combining Squares

Lecture 3

- By combining squares, we reduce number of literals in a product term, reducing the literal cost, thereby reducing the other two cost criteria
- On a 3-variable K-Map:
 - One square represents a minterm with three variables
 - Two adjacent squares represent a product term with two variables (apply identities 7,14 **one time**)
 - Four “adjacent” terms represent a product term with one variable (apply identities 7,14 **three times**)
 - Eight “adjacent” terms is the function of all ones (no variables) = 1. (apply identities 7,14 **seven times**)

 




Combining Squares: Example

Lecture 3

- Example: Let $F = \Sigma m(2,3,6,7)$
- | | | | | |
|----------|----|----|-------------|-----|
| | | | y | |
| | 0 | 1 | 3 1 | 2 1 |
| x | 4 | 5 | 7 1 | 6 1 |
| | 00 | 01 | z 11 | 10 |
- Applying the Minimization Theorem three times:

$$\begin{aligned} F(x, y, z) &= \bar{x}yz + xyz + \bar{x}y\bar{z} + xy\bar{z} \\ &= yz + y\bar{z} \\ &= y \end{aligned}$$

 - Thus the four terms that form a 2×2 square correspond to the term "y".







Three-Variable Maps (1/4)

Lecture 3

  - Topological warps of 3-variable K-maps that show *all* adjacencies:
 - Venn Diagram







Three-Variable Maps (2/4)

Lecture 3

- Example Shapes of 2-cell Rectangles:

 

 - Read off the product terms for the rectangles shown







Three-Variable Maps (3/4)

Lecture 3

- Example Shapes of 4-cell Rectangles:

 

 
- Read off the product terms for the rectangles shown






Three Variable Maps (4/4)

 - K-Maps can be used to simplify Boolean functions by systematic methods. Terms are selected to cover the “1s” in the map.
- Example: Simplify $F(x, y, z) = \Sigma_m(1,2,3,5,7)$



$$F(x, y, z) = z + \bar{x} y$$

 





Three-Variable Map Simplification

Lecture 3

 - Use a K-map to find an optimum SOP equation for $F(X, Y, Z) = \Sigma_m(0,1,2,4,6,7)$




 
$$F = \overline{X}\overline{Y} + XY + \overline{Z}$$





Four Variable Maps


- Map and location of minterms:

 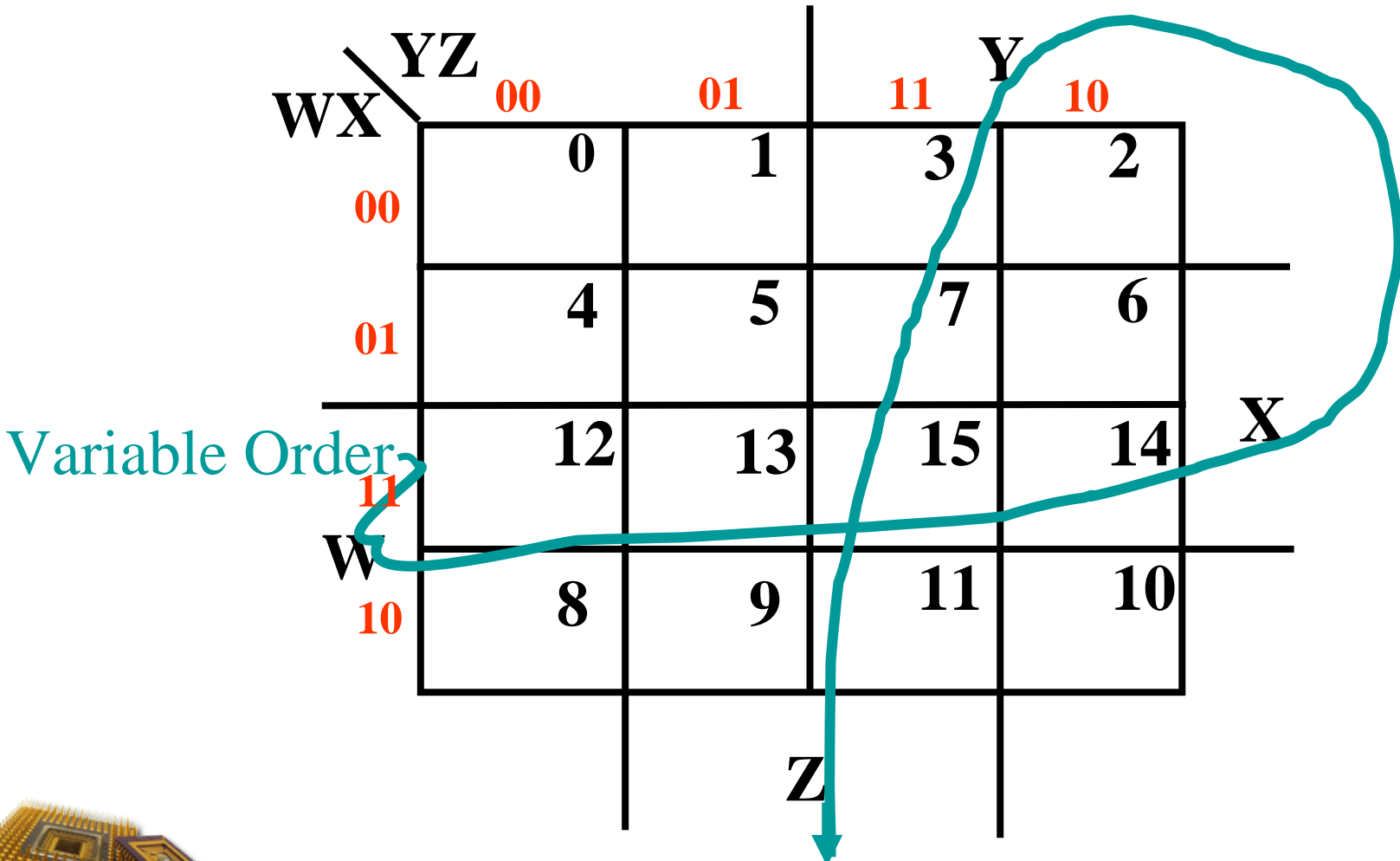



Four Variable Terms


 
- Four variable maps can have rectangles corresponding to:
 - A single 1 = 4 variables, (i.e. Minterm)
 - Two 1s = 3 variables,
 - Four 1s = 2 variables
 - Eight 1s = 1 variable,
 - Sixteen 1s = zero variables (i.e. Constant "1")





Four-Variable Maps



- Example Shapes of Rectangles:

  



Four-Variable Maps

- Example Shapes of Rectangles:

 
 




Four-Variable Map Simplification (1/2)

Lecture 3

 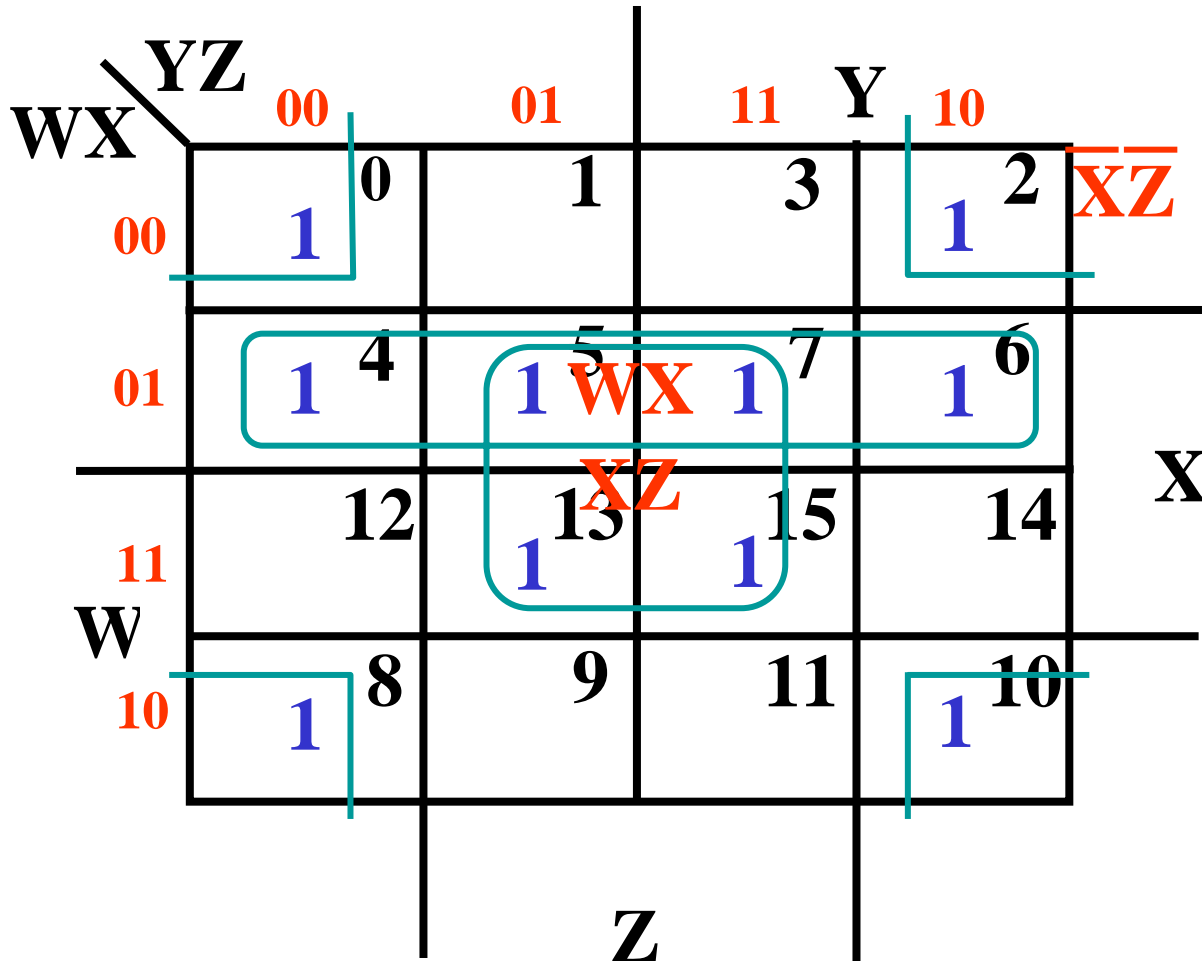■ $F(W, X, Y, Z) = \Sigma_m(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$







Four-Variable Map Simplification (2/2)

Lecture 3

  - $F(W, X, Y, Z) = \Sigma_m(3, 4, 5, 7, 9, 13, 14, 15)$






Systematic Simplification

Lecture 3

- *Implicant* – a product term of which if the function has the value 1 for all minterms.
- A *Prime Implicant* is a product term obtained by combining the maximum possible number of adjacent squares in the map into a rectangle with the number of squares a power of 2 – remove any literal → not a implicant.
- A prime implicant is called an *Essential Prime Implicant* if it is the only prime implicant that covers (includes) one or more minterms.
- Prime Implicants and Essential Prime Implicants can be determined by inspection of a K-Map.
- A set of prime implicants "*covers all minterms*" if, for each minterm of the function, at least one prime implicant in the set of prime implicants includes the minterm.


 




Example of Prime Implicants

Lecture 3

- Find ALL Prime Implicants

 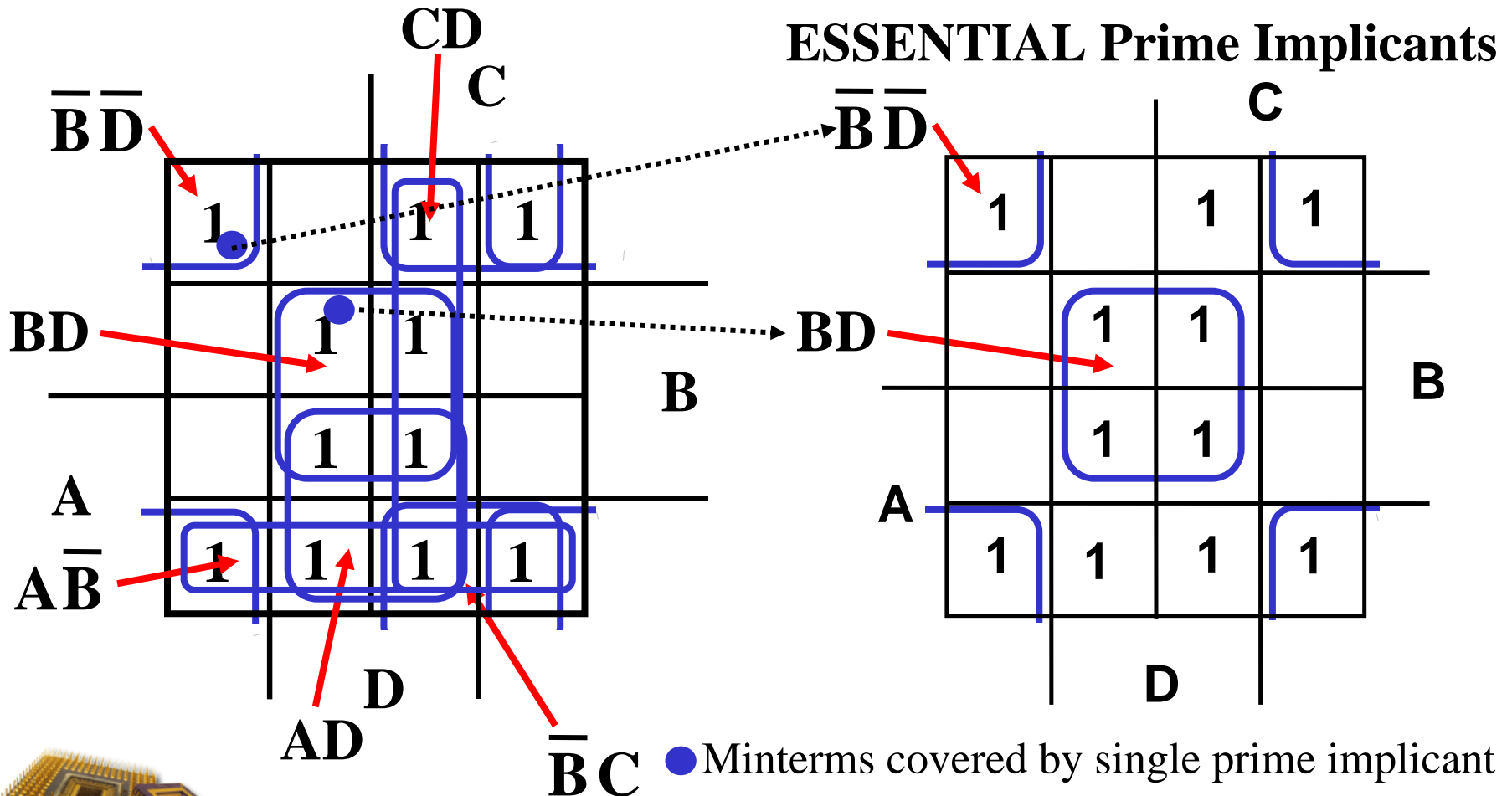





Prime Implicant Practice

Lecture 3

- Find all prime implicants for:
  
$$F(A, B, C, D) = \sum_m(0, 2, 3, 8, 9, 10, 11, 12, 13, 14, 15)$$







Another Example

- Find all prime implicants for:

$$G(A, B, C, D) = \sum_m(0, 2, 3, 4, 7, 12, 13, 14, 15)$$

  - Hint: There are seven prime implicants!






Five Variable or More K-Maps

Lecture 3

 - For five variable problems, we use *two adjacent K-maps*. It becomes harder to visualize adjacent minterms for selecting PIs. You can extend the problem to six variables by using four K-Maps.






Prime Implicants Selection Rule

Lecture 3


- Find all prime implicants.
- Include all essential prime implicants in the solution
- Select a minimum cost set of non-essential prime implicants to cover all minterms not yet covered:
 - Minimize the overlap among prime implicants as much as possible.
 - Make sure that each prime implicant selected includes at least one minterm not included in any other prime implicant selected – avoid redundancy.

 




Selection Rule Example

 - Simplify $F(A, B, C, D)$ given on the K-map.



 ✓ Minterms covered by essential prime implicants






Product-of-Sums Simplification


Lecture 3

 - Concept: $\overline{m}_i = M_i$
- How to derive a POS using SOP derivation:
 - Derive $\overline{F} = m_i + m_j + \dots + m_n \leftrightarrow F = M_i \cdot M_j \dots \cdot M_n$



$$\overline{F} = AB + CD + B\overline{D}$$
 
$$F = (\overline{A} + \overline{B})(\overline{C} + \overline{D})(\overline{B} + D)$$






Product-of-Sums Simplification

Lecture 3

- How to derive a simplified SOP and POS from a POS?

$$F = (\bar{A} + C + D)(\bar{A} + C + \bar{D})(A + \bar{B} + \bar{D})(\bar{A} + \bar{B} + \bar{D})$$

 
$$\bar{F} = A\bar{C}\bar{D} + A\bar{C}D + \bar{A}BD + ABD$$



$$F = \bar{A}\bar{B} + C\bar{D} + \bar{A}\bar{D} + \bar{B}C$$

$$\bar{F} = A\bar{C} + BD$$

$$F = (\bar{A} + C)(\bar{B} + \bar{D})$$

 




Don't Cares in K-Maps

Lecture 3

- Sometimes a function table or map contains entries for which it is known:
 - the input values for the minterm will never occur, or
 - The output value for the minterm is not used
- In these cases, the output value need not be defined
 - Incompletely specified functions – functions that have unspecified outputs (it can be 1 or 0) for some input combinations.
- Instead, the output value is defined as a “don't care”
- By placing “don't cares” (an “x” entry) in the function table or map, the cost of the logic circuit may be lowered.
- Example 1: A logic function having the binary codes for the BCD digits as its inputs. Only the codes for 0 through 9 are used. The six codes, 1010 through 1111 never occur, so the output values for these codes are “x” to represent “don't cares.”

 




 Example: BCD “5 or More”

Lecture 3

- The map below gives a function $F1(w,x,y,z)$ which is defined as "5 or more" over **BCD inputs**. With the don't cares used for the 6 non-BCD combinations:




$$F1(w,x,y,z) = \bar{w}xz + \bar{w}xy + w\bar{x}\bar{y} \quad G = 12$$

- Consider the input characteristics

$$F2(w,x,y,z) = w + xz + xy \quad G = 7$$

 
- This is much lower in cost than $F2$ where the “don't cares” were treated as “0s.”






Don't Care – Another Example

Lecture 3

 


$$F = CD + \bar{A}\bar{B}$$

 

$$\bar{F} = \bar{D} + A\bar{C}$$

$$F = D(\bar{A} + C)$$

$$F = CD + \bar{A}D$$

 





Selection Rule Example with Don't Cares

Lecture 3

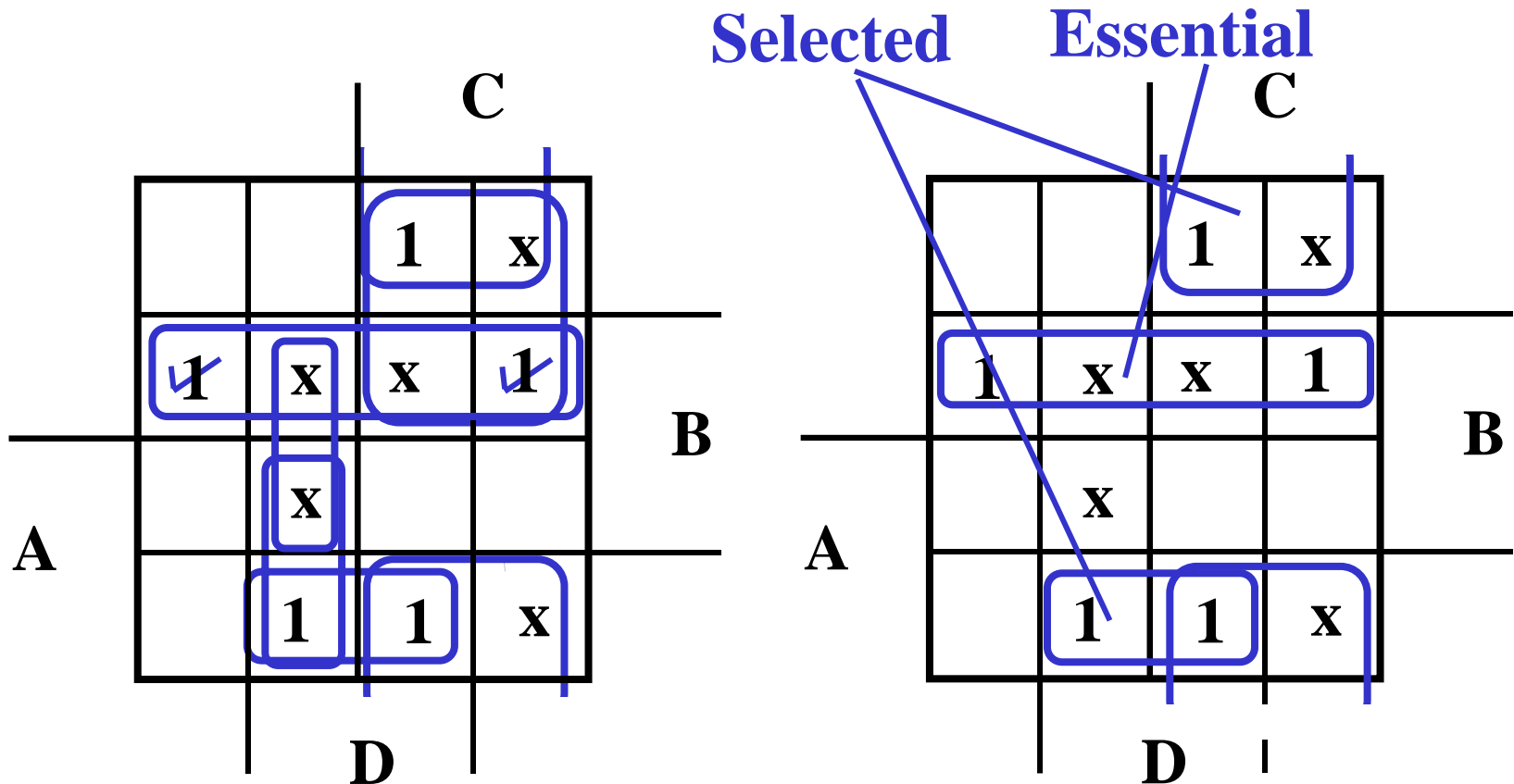- Simplify $F(A, B, C, D)$ given on the K-map.



 ✓ Minterms covered by essential prime implicants






Example: Product of Sums

Lecture 3

- Find the optimum POS solution:


$$F(A, B, C, D) = \Sigma_m(3, 9, 11, 12, 13, 14, 15) + \Sigma_d(1, 4, 6)$$

 - Hint: Use \bar{F} and complement it to get the result.



$$\bar{F} = \bar{A}B + \bar{B}\bar{D}$$

$$F = (A + \bar{B})(B + D)$$

 



Multiple-Level Optimization

Lecture 3


- Multiple-level circuits - circuits that are not two-level (with or without input and/or output inverters)
- Multiple-level circuits can have reduced gate input cost compared to two-level (SOP and POS) circuits
- Multiple-level optimization is performed by applying transformations to circuits represented by equations while evaluating cost

$$F = ABC + ABD + AB\overline{C}\overline{D}$$

2 levels, 4 gates, 13 gate inputs

$$F = AB(C + D + \overline{C}\overline{D})$$


3 levels, 3 gates, 8 gate inputs

 



Transformations

 - Factoring - finding a factored form from SOP or POS expression
- Decomposition - expression of a function as a set of new functions
- Substitution of G into F - expression function F as a function of G and some or all of its original variables
- Elimination - Inverse of substitution
- Extraction - decomposition applied to multiple functions simultaneously





Transformation Examples (1/6)

Lecture 3

- Algebraic Factoring

$$F = \bar{A} \bar{C} \bar{D} + \bar{A} B \bar{C} + ABC + AC \bar{D} \quad G = 16$$

- Factoring:


$$F = \bar{A} (\bar{C} \bar{D} + B \bar{C}) + A (BC + C \bar{D}) \quad G = 18$$

- Factoring again:

$$F = \bar{A} \bar{C} (B + \bar{D}) + AC (B + \bar{D}) \quad G = 12$$

- Factoring again:
 
$$F = (\bar{A} \bar{C} + AC) (B + \bar{D}) \quad G = 10$$





Transformation Examples (2/6)


Lecture 3

■ Decomposition

- The terms $B + \bar{D}$ and $\bar{A}\bar{C} + AC$ can be defined as new functions E and H respectively, decomposing F :

$$F = E H, E = B + \bar{D}, \text{ and } H = \bar{A}\bar{C} + AC \quad G = 10$$

 - This series of transformations has reduced G from 16 to 10, a substantial savings. The resulting circuit has three levels plus input inverters.





Transformation Examples (3/6)

Lecture 3

■ Substitution of E into F

- Returning to F just before the final factoring step:


$$F = \bar{A}\bar{C}(B + \bar{D}) + AC(B + \bar{D}) \quad G = 12$$

- Defining $E = B + \bar{D}$, and substituting in F:



$$F = \bar{A}\bar{C}E + ACE \quad G = 10$$

- This substitution has resulted in the same cost as the decomposition
 
$$F = \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C} + ABC + AC\bar{D}$$


  
$$F = \bar{A}\bar{C}E + ACE, \quad E = B + \bar{D}$$





Transformation Examples (4/6)

Lecture 3

■ Elimination

- Beginning with a new set of functions:

$$X = B + C$$

$$Y = A + B$$

$$Z = \bar{A}X + C Y \quad G = 10$$


- Eliminating X and Y from Z :

$$Z = \bar{A}(B + C) + C (A + B) \quad G = 10$$

- “Flattening” (Converting to SOP expression):

$$Z = \bar{A} B + \bar{A} C + AC + BC \quad G = 12$$

 - This has increased the cost, but has provided an new SOP expression for two-level optimization.





Transformation Examples (5/6)

Lecture 3


■ Two-level Optimization

- The result of 2-level optimization is:

$$Z = \bar{A}B + C \qquad G = 4$$

■ This example illustrates that:

 - Optimization can begin with any set of equations, not just with minterms or a truth table
- Increasing gate input count G temporarily during a series of transformations can result in a final solution with a smaller G





Transformation Examples (6/6)

Lecture 3

■ Extraction

- Beginning with two functions:

$$E = \bar{A}\bar{B}\bar{D} + \bar{A}BD$$

$$H = \bar{B}C\bar{D} + BCD$$

$$G = 16$$


- Finding a common factor and defining it as a function:

$$F = \bar{B}\bar{D} + BD$$

- We perform extraction by expressing E and H as the three functions:

$$F = \bar{B}\bar{D} + BD, E = \bar{A}F, H = CF \quad G = 10$$

 
- The reduced cost G results from the sharing of logic between the two output functions





Universal

 - A set of gates is said to be universal if any Boolean function can be composed of the elements of this set.
 - {AND, OR, NOT} – a universal set.
- Universal gate - a gate type that can implement any Boolean function.
 - NAND, NOR,...






Other Gate Types

Lecture 3


- Why?
 - Implementation feasibility and low cost
 - Power in implementing Boolean functions
 - Convenient conceptual representation
- Gate classifications
 - Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion(s).
 - Complex gate - a gate that requires more than one primitive operation type for its description (XOR, XNOR).
- Primitive gates will be covered first.

 




Buffer

 - A buffer is a gate with the function $F = X$:



 
- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.






NAND Gate (1/3)

 - The basic NAND gate has the following symbol, illustrated for three inputs:
 - AND-Invert (NAND)



 
- NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle (“bubble”) represents the invert function.






NAND Gates (2/3)

 - Applying DeMorgan's Law gives Invert-OR (NAND)






 
- This NAND symbol is called **Invert-OR**, since inputs are inverted and then ORed together.
- AND-Invert and Invert-OR both represent the NAND gate. Having both makes visualization of circuit function easier.
- A NAND gate with one input degenerates to an inverter.





NAND Gates (3/3)

    - The NAND gate is the natural implementation for the simplest and fastest electronic circuits
- The NAND gate is a universal gate as shown in the following.
- NAND usually does not have an operation symbol defined since
 - the NAND operation is not associative, and
 - we have difficulty dealing with non-associative mathematics!









Two-level NAND Gates (1/2)

Lecture 3

- A function of sum-of-products form is easy to convert to NAND gates.

    - $F = AB + CD \rightarrow F = \overline{\overline{AB + CD}} \rightarrow F = \overline{\overline{AB}} \cdot \overline{\overline{CD}}$







Multilevel NAND Gates (2/2)

Lecture 3

  
- The procedures to convert to multilevel NAND gates circuits:
 - Convert all AND gates to NAND gates with **AND-NOT** graphic symbols.
 - Convert all OR gates to NAND gates with **NOT-OR** graphic symbols.
 - Complement the input literal if the signal has single bubble, and insert a NOT gate for the output signal with single bubble.






NOR Gate (1/4)

 - The basic NOR gate has the following symbol, illustrated for three inputs:
 - OR-Invert (NOR)



 
- NOR represents NOT-OR, i. e., the OR function with a NOT applied. The symbol shown is an **OR-Invert**. The small circle (“bubble”) represents the invert function.






NOR Gate (2/4)

 - Applying DeMorgan's Law gives Invert-AND (NOR)






 
- This NOR symbol is called Invert-AND, since inputs are inverted and then ANDed together.
- OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- A NOR gate with one input degenerates to an inverter.





NOR Gate (3/4)

    - The NOR gate is another natural implementation for the simplest and fastest electronic circuits
- The NOR gate is a universal gate
- NOR usually does not have a defined operation symbol since
 - the NOR operation is not associative, and
 - we have difficulty dealing with non-associative mathematics!







NOR Gate (4/4)

Lecture 3


■ Example:

  



XOR/XNOR (1/4)


- The *eXclusive OR* (*XOR*) function is an important Boolean function used extensively in logic circuits.
- The XOR function may be;
 - implemented directly as an electronic circuit (truly a gate) or
 - implemented by interconnecting other gate types (used as a convenient representation)
- The *eXclusive NOR* function is the complement of the XOR function
- By our definition, XOR and XNOR gates are complex gates.

 



XOR/XNOR (2/4)

- Uses for the XOR and XNORs gate include:
 - Adders/subtractors/multipliers
 - Counters/incrementers/decrementers
 - Parity generators/checkers
- Definitions
 - The XOR function is: $X \oplus Y = X \bar{Y} + \bar{X} Y$
 - The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is: $\overline{X \oplus Y} = X Y + \bar{X} \bar{Y}$
- Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

 



XOR/XNOR (3/4)


- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

X	Y	$\overline{(X \oplus Y)}$ or $X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

 - The XOR function means:
X OR Y, but NOT BOTH
- Why is the XNOR function also known as the *equivalence* function, denoted by the operator \equiv ?
<XNOR (X, X)=1>





XOR/XNOR (4/4)

- The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum (Mod 2 sum)*, not an XOR:

$$X \oplus Y \oplus Z = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

- The complement of the odd function is the even function.
- The XOR identities:

$$X \oplus 0 = X$$


$$X \oplus 1 = \bar{X}$$

$$X \oplus X = 0$$

$$X \oplus \bar{X} = 1$$

$$X \oplus Y = Y \oplus X$$
 
$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$







Symbols For XOR and XNOR

Lecture 3


- XOR symbol:

 

- XNOR symbol:

 

- Symbols exist only for two inputs

 




XOR Implementations

Lecture 3



- The simple SOP implementation uses the following structure:
 
$$\begin{aligned}x\bar{y} &= x\bar{y} + x\bar{x} \\ &= x(\bar{x} + \bar{y}) \\ &= x\bar{x}\bar{y}\end{aligned}$$



- A NAND only implementation is:
  
$$\begin{aligned}y\bar{x} &= y\bar{x} + y\bar{y} \\ &= y(\bar{x} + \bar{y}) \\ &= y\bar{x}\bar{y}\end{aligned}$$






Odd and Even Functions

- The odd and even functions on a K-map form “checkerboard” patterns.
- The 1s of an odd function correspond to minterms having an index with an odd number of 1s.
- The 1s of an even function correspond to minterms having an index with an even number of 1s.
- Implementation of odd and even functions for greater than 4 variables as a two-level circuit is difficult, so we use “trees” made up of :
 - 2-input XOR or XNORs
 - 3- or 4-input odd or even functions

	00	01	11	10
00	E	O	E	O
01	O	E	O	E
11	E	O	E	O
10	O	E	O	E


 




  Example: Odd Function Implementation

Lecture 3

- Design a 4-input odd function $F = X \oplus Y \oplus Z \oplus W$ with 2-input XOR gates
- Factoring, $F = (X \oplus Y) \oplus Z \oplus W$
- The circuit:







  Example: Even Function Implementation

Lecture 3

- Design a 4-input even function $F = \overline{W \oplus X \oplus Y \oplus Z}$ with 2-input XOR and XNOR gates
- Factoring, $F = \overline{(W \oplus X) \oplus (Y \oplus Z)}$
- The circuit:






Hi-Impedance Outputs (1/2)

Lecture 3

- Logic gates introduced thus far
 - have 1 and 0 output values,
 - cannot have their outputs connected together, and
 - transmit signals on connections in only one direction.
- Three-state logic adds a third logic value, Hi-Impedance (Hi-Z), giving three states: 0, 1, and Hi-Z on the outputs.
- The presence of a Hi-Z state makes a gate output as described above behave quite differently:
 - “1 and 0” become “1, 0, and Hi-Z”
 - “cannot” becomes “can,” and
 - “only one” becomes “two”

 




Hi-Impedance Outputs (2/2)

Lecture 3


- What is a Hi-Z value?
 - The Hi-Z value behaves as an open circuit
 - This means that, looking back into the circuit, the output appears to be disconnected.
 - It is as if a switch between the internal circuitry and the output has been opened.
- Hi-Z may appear on the output of any gate, but we restrict gates to:
 - a 3-state buffer, or
 - a transmission gate,each of which has one data input and one control input.

 




3-State Buffer

 - For the symbol and truth table, IN is the data input, and EN, the control input.
- For $EN = 0$, regardless of the value on IN (denoted by X), the output value is Hi-Z.
- For $EN = 1$, the output value follows the input value.
- Variations:
 - Data input, IN, can be inverted
 - Control input, EN, can be inverted by addition of “bubbles” to signals.



Truth Table

EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

 




Resolving 3-State Values on a Connection

Lecture 3

- Connection of two 3-state buffer outputs, B1 and B0, to a wire, OUT
- Assumption: Buffer data inputs can take on any combination of values 0 and 1
- Resulting Rule: At least one buffer output value must be Hi-Z. Why?
- How many valid buffer output combinations exist?
- What is the rule for n 3-state buffers connected to wire, OUT?
- How many valid buffer output combinations exist?

Resolution Table		
B1	B0	OUT
0	Hi-Z	0
1	Hi-Z	1
Hi-Z	0	0
Hi-Z	1	1
Hi-Z	Hi-Z	Hi-Z


 




3-State Logic Circuit

- Data Selection Function: If $s = 0$, $OL = IN0$, else $OL = IN1$
- Performing data selection with 3-state buffers:
- Since $EN0 = S$ and $EN1 = \bar{S}$, one of the two buffer outputs is always Hi-Z plus the last row of the table never occurs.






EN1	EN0	IN1	IN0	OL
0	0	X	X	Hi-Z
(S) 0	(\bar{S}) 1	X	0	0
0	1	X	1	1
1	0	0	X	0
1	0	1	X	1
1	1	0	0	0
1	1	1	1	1
1	1	0	1	
1	1	1	0	

  



Transmission Gates (1/2)

     - The transmission gate is one of the designs for an electronic switch for connecting and disconnecting two points in a circuit:






Transmission Gates (2/2)

Lecture 3

- In many cases, X can be regarded as a data input and Y as an output. C and \overline{C} , with complementary values applied, is a control input.
- With these definitions, the transmission gate, provides a 3-state output:
 - $C = 1, Y = X$ ($X = 0$ or 1)
 - $C = 0, Y = \text{Hi-Z}$
- Care must be taken when using the TG in design, however, since X and Y as input and output are interchangeable, and signals can pass in both directions.

 




Circuit Example Using TG

Lecture 3

- Exclusive OR $F = A \oplus C$

 


(a)

A	C	TG1	TG0	F
0	0	No path	Path	0
0	1	Path	No path	1
1	0	No path	Path	1
1	1	Path	No path	0

(b)

 - The basis for the function implementation is TG-controlled paths to the output





Terms of Use

Lecture 3

- © 2004 by Pearson Education, Inc. All rights reserved.
- The following terms of use apply in addition to the standard Pearson Education [Legal Notice](#).
- Permission is given to incorporate these materials into classroom presentations and handouts only to instructors adopting Logic and Computer Design Fundamentals as the course text.
- Permission is granted to the instructors adopting the book to post these materials on a protected website or protected ftp site in original or modified form. All other website or ftp postings, including those offering the materials for a fee, are prohibited.
- You may not remove or in any way alter this Terms of Use notice or any trademark, copyright, or other proprietary notice, including the copyright watermark on each slide.
- [Return to Title Page](#)

